


* Block Diagram of n-bit parallel Adder.

The full adder consists of three inputs (A, B, Cin) & two outputs (Cout, sum).

A n-bit parallel adder can be using no. of full adder circuits connected in parallel i.e the carry output of each adder is connected to the carry input of the next higher-order adder.

→ Carry input of a full-adder is made 0 because there is no carry into the least significant bit position.

Parallel Subtractor :-

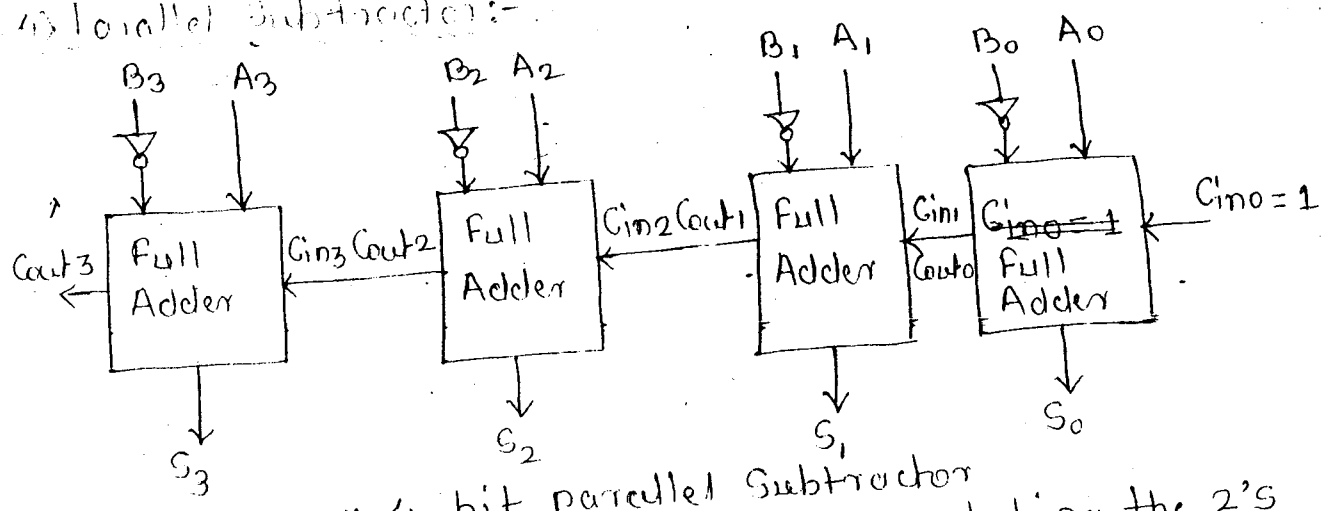

* 4-bit parallel Subtractor


→ The subtraction $A - B$ can be done by taking the complement of B & adding it to A.

→ The 2's complement can be obtained by taking the 1's complement & adding one to the least significant pair of bits.

→ The 1's complemented can be implemented with inverters & a one can be added to the sum through the input carry.

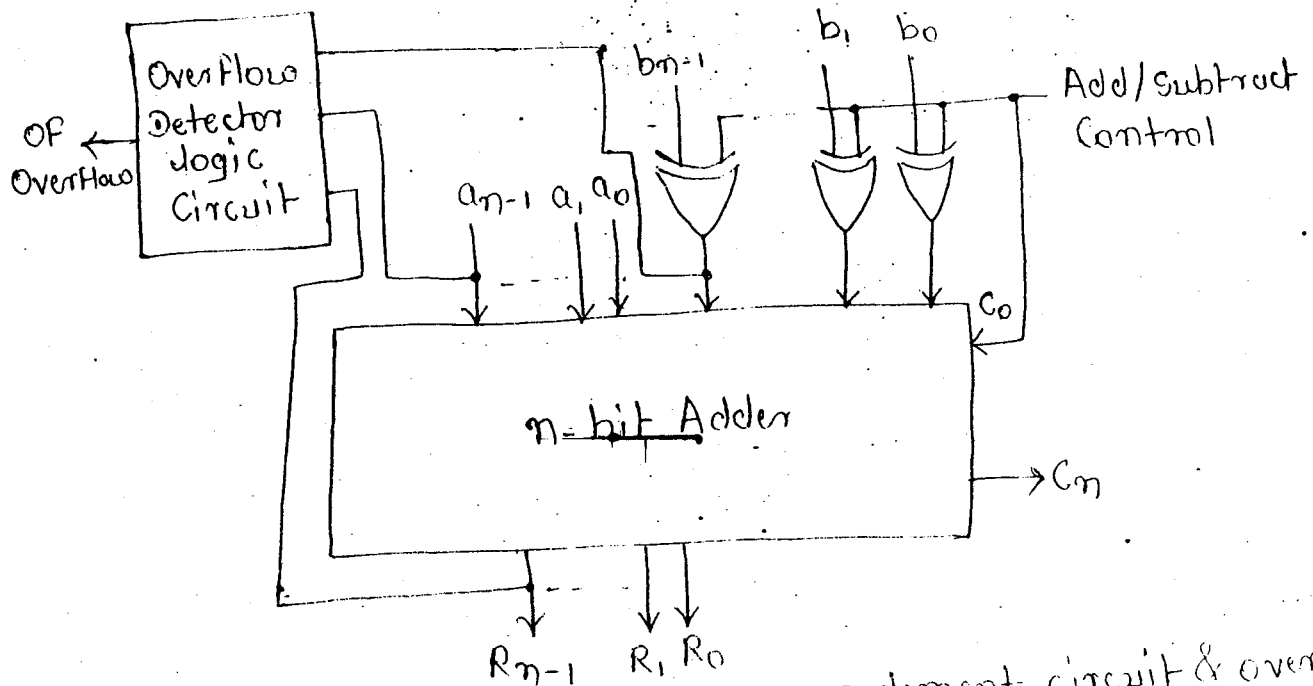5) Parallel Adder/Subtractor with overflow


* Hardware for integer addition & subtraction:



- It consists of n-bit adder, 2's complement circuit & overflow detector logic circuit.
- Number a & Number b are the two inputs for n-bit adder.
- For subtraction the number b is converted into its 2's complement form by making Add/Subtract control signal to the logic 1.
- When Add/Subtract control signal is one all bits of number b are complemented & carry zero is set to 1.
- ∴ n-bit adder gives result as $R = a + \bar{b} + 1$
- where $\bar{b} + 1$ represents 2's complement of number b.

* Overflow detector logic circuit:
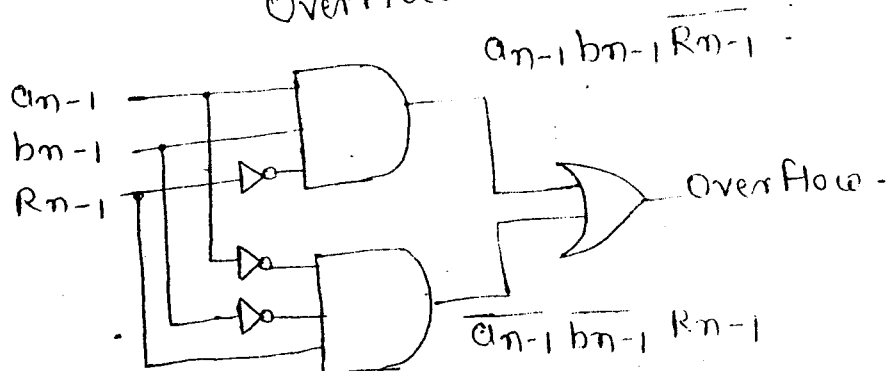
$$\text{Overflow} = a_{n-1} b_{n-1} R_{n-1} + \overline{a_{n-1}} \overline{b_{n-1}} \overline{R_{n-1}}$$



Carry Propagation delay: The sum & carry outputs of any stage cannot be produced until the input carry occurs, this leads to a time delay in the addition process. This delay is known as Carry Propagation delay.


for ex:-

$$\begin{array}{r} 0101 \\ + 0011 \\ \hline 1000 \end{array}$$

Speeding up this process by eliminating inter stage carry delay is called Carry Look Ahead Adder.

It uses two functions: Carry generate & Carry propagate

→ Full-adder Circuit:

 

We define two functions: Carry generate (G_i) & carry propagate (P_i)

$$P_i = A_i \oplus B_i = A_i \bar{B}_i + \bar{A}_i B_i$$

$$G_i = A_i B_i$$

The output Sum (S_i):

$$S_i = P_i \oplus C_i = P_i \bar{C}_i + C_i P_i$$

$$C_{i+1} = G_i + P_i C_i$$

$$= A_i B_i + (A_i \oplus B_i) C_i$$

$$= A_i B_i + (\bar{A}_i B_i + A_i \bar{B}_i) C_i$$

$$= A_i B_i + \bar{A}_i B_i C_i + A_i \bar{B}_i C_i$$

$$= A_i B_i (C_{i+1}) + \bar{A}_i B_i C_i + A_i \bar{B}_i C_i \quad (\because C_{i+1} = 1)$$

$$\begin{aligned}
&= A_i B_i C_i + A_i B_i + \bar{A}_i B_i C_i + A_i \bar{B}_i C_i \\
&= A_i B_i (C_i + 1) \\
&= A_i B_i + A_i C_i (B_i + \bar{B}_i) + \bar{A}_i B_i C_i \\
&= A_i B_i + A_i C_i + \bar{A}_i B_i C_i \\
&= A_i B_i + A_i C_i + \bar{A}_i B_i C_i \\
&= A_i B_i (C_i + 1) + A_i C_i + \bar{A}_i B_i C_i \\
&= A_i B_i C_i + A_i B_i + A_i C_i + \bar{A}_i B_i C_i \\
&= B_i C_i (A_i + \bar{A}_i) + A_i B_i + A_i C_i
\end{aligned}$$

$$\boxed{C_{i+1} = A_i B_i + A_i C_i + B_i C_i} \quad C_{i+1} = A_i B_i + (A_i + B_i) C_i$$

$$\therefore \boxed{C_{i+1} = G_i + P_i C_i} \quad \text{--- Carry} \quad \therefore P_i = (A_i + B_i)$$

$$S_i = P_i \oplus C_i$$

$$= P_i \oplus C_i = (A_i \oplus B_i) \oplus C_i$$

$$= [A_i \bar{B}_i + B_i \bar{A}_i] \oplus C_i$$

$$= P_i \bar{C}_i + \bar{P}_i C_i$$

$$= (A_i \oplus B_i) \bar{C}_i + \overline{(A_i \oplus B_i)} C_i$$

$$= (A_i \bar{B}_i + \bar{A}_i B_i) \bar{C}_i + (A_i \odot B_i) C_i$$

$$= A_i \bar{B}_i \bar{C}_i + \bar{A}_i B_i \bar{C}_i + (A_i B_i + \bar{A}_i \bar{B}_i) C_i$$

$$\boxed{S_i = A_i \bar{B}_i \bar{C}_i + \bar{A}_i B_i \bar{C}_i + A_i B_i C_i + \bar{A}_i \bar{B}_i C_i}$$

$$\boxed{S_i = P_i \oplus C_i}$$

G_i : Carry generate & it produces an carry when both A_i & B_i are one, regardless of the input carry.


P_i : Carry propagate because it is term associated with the propagation of the carry from C_i to C_{i+1} .

C_{i+1} : Sum of products function of the P & C outputs of all the preceding stages.

Carry-look ahead adder can be expressed as:

$$C_1 = G_0 + P_0 C_{in}$$
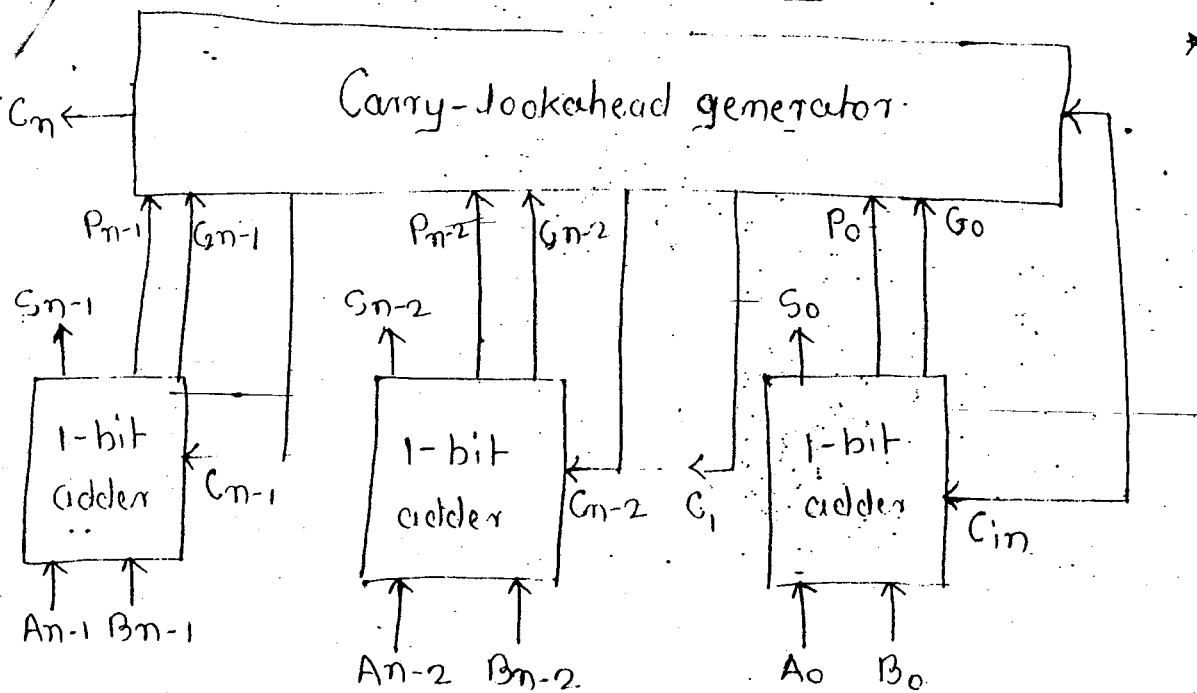
$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_{in}$$



* Carry lookahead adder circuit

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{in}$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_{in}$$

Let us assume,

$$S_i = P_i \oplus G_i \oplus C_i$$

$$P_i = A_i + B_i$$

$$G_i = A_i B_i$$

$$S_i = (A_i + B_i) \oplus A_i B_i \oplus C_i$$

$$= \left[\overline{(A_i + B_i)} (A_i B_i) + (A_i + B_i) \overline{(A_i B_i)} \right] \oplus C_i$$


$$= \left[\overline{A_i B_i} (A_i B_i) + (A_i + B_i) (\overline{A_i} + \overline{B_i}) \right] \oplus C_i$$

$$= \left[0 + A_i \overline{A_i} + A_i \overline{B_i} + B_i \overline{A_i} + B_i \overline{B_i} \right] \oplus C_i$$


$$= (A_i \overline{B_i} + B_i \overline{A_i}) \oplus C_i$$

$$S_i = A_i \oplus B_i \oplus C_i$$

Carry-lookahead circuit:
(4-bit)

 


Manual multiplication Algorithm:

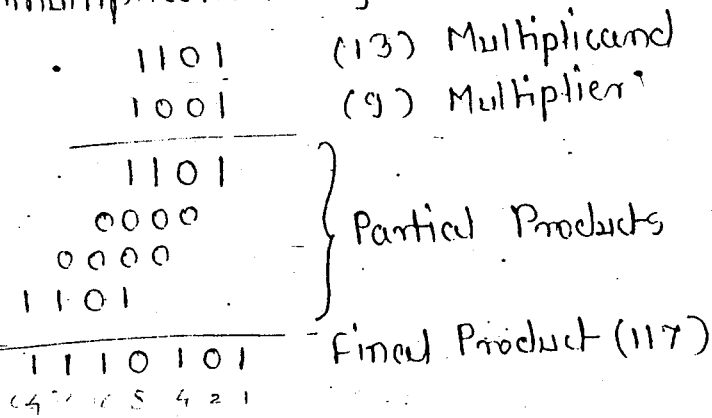

- 1) Multiplication process involves generation of partial products, one for each digit in the multiplier. These partial products are then summed to produce the final product.
- 2) In the binary system the partial products can be defined as: When the multiplier bit is 0, the partial product is 0, & when the multiplier bit is 1, the partial product is the multiplicand.
- 3) The final product is produced by summing the partial products. Before summing operation each successive partial product is shifted one position to the left relative to the preceding partial product.
- 4) The product of 2ⁿ-digit no. can be 2ⁿ digits.

Implementation of manual multiplication:

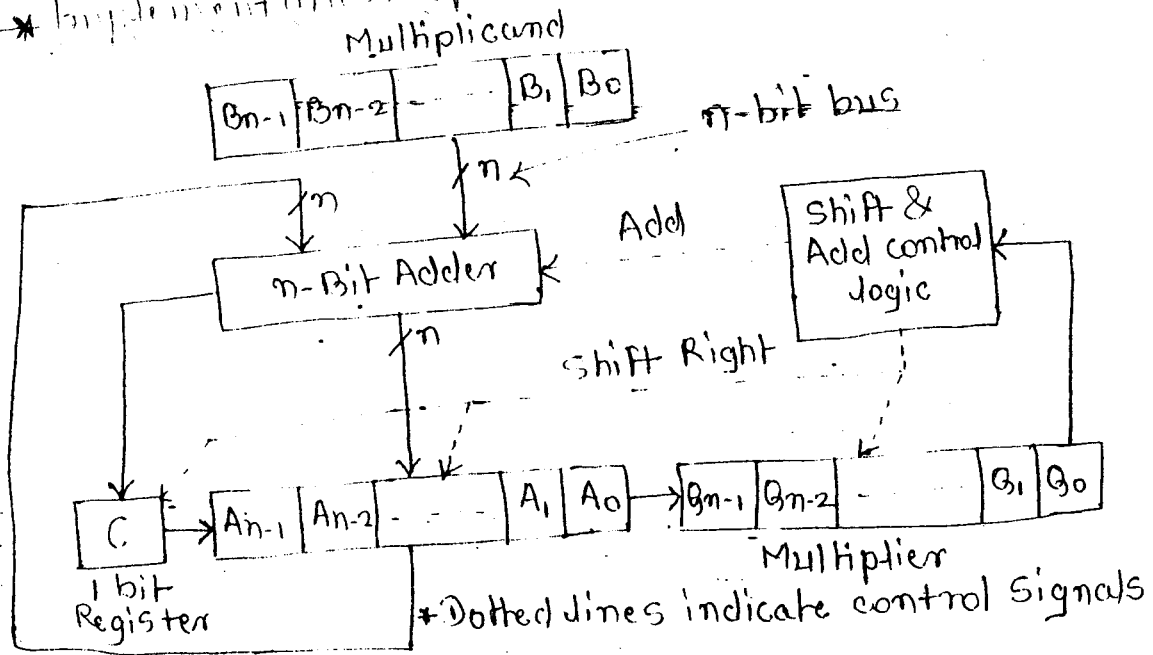

* Dotted lines indicate control signals.

Multiplication Operation Steps:


It consists of n -bit binary adder, shift & add control logic & four registers, A, B, C & Q. Multiplier & Multiplicand are loaded into register Q & register B. & C are initially set to 0.

1) IF bit 0 (Q_0) is one then multiplicand & partial product are added & all bits of C, A & Q registers are shifted to the right one bit, so that the C -bit goes into A_{n-1} , A_0 goes into Q_{n-1} , & Q_0 is lost.

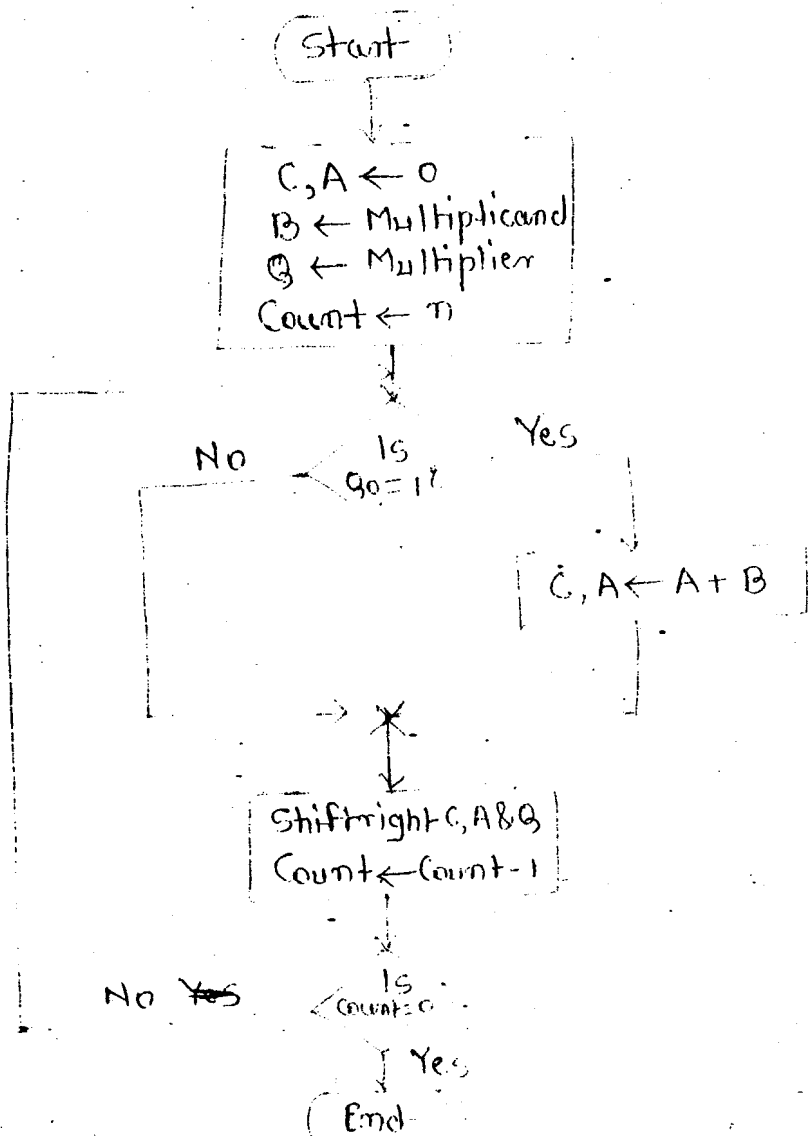2) IF bit 0 (Q_0) is 0, then no addition is performed, only shift operation is carried out.

∴ Similarly steps 1 & 2 repeated n -times.

* Flowchart for multiplication operation:




of example:-

consider 4-bit multiplier & multiplicand:

(~~Q~~) Multiplier = 1101 & (~~Q~~) Multiplier = 1011

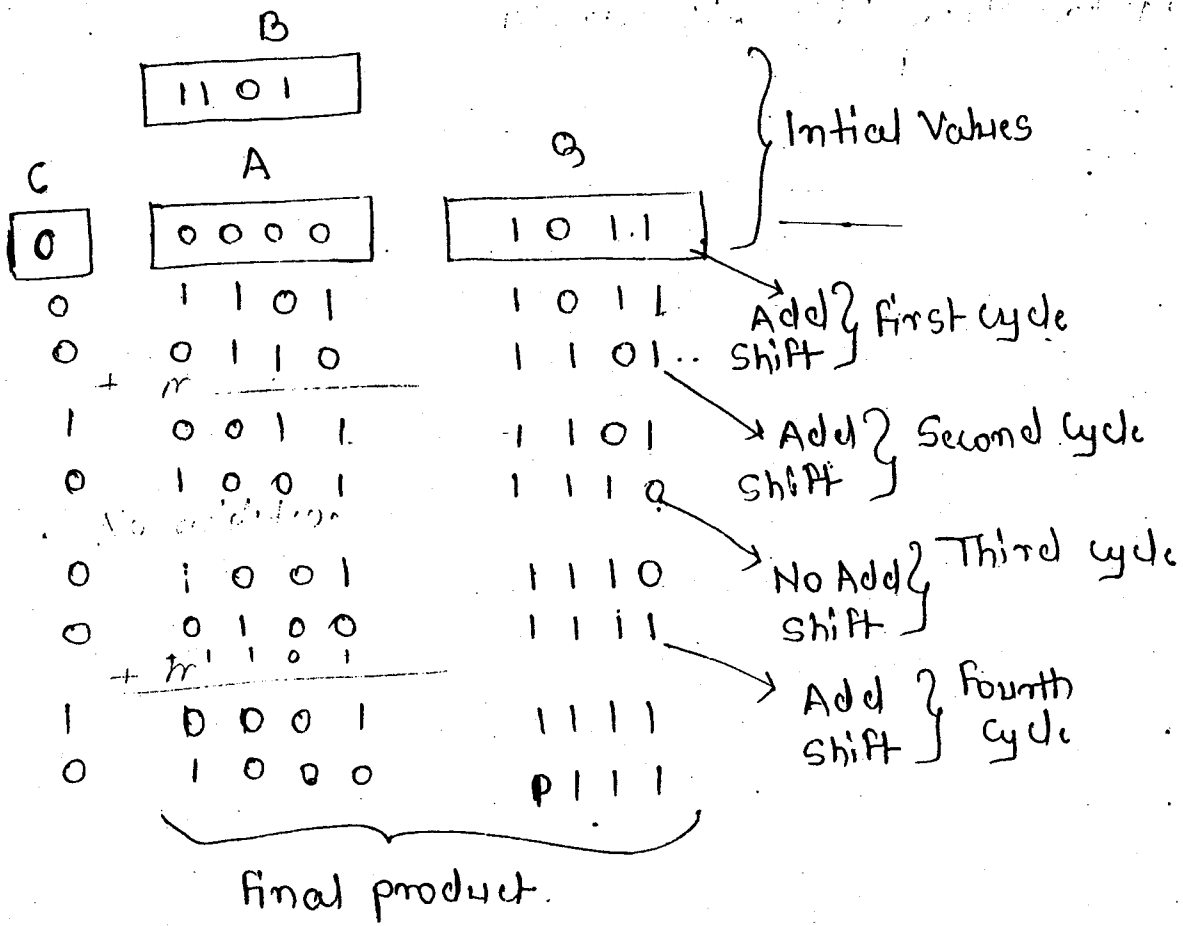(~~B~~) Multiplicand = 1011 & (~~B~~) Multiplicand = 1101



Booth's Algorithm:-

A powerful algorithm for signed-number multiplication is a Booth's algorithm, which generates a 2n-bit product & treats both positive & negative numbers uniformly.

Booth multiplier recoding table:

Multiplier Bit i	Multiplier Bit i-1	Version of Multiplicand Selected by bit i
0	0	0xM
0	1	+1xM
1	0	-1xM
1	1	0xM

ex:- Recode the multiplier 101100 for booth's multiplication:

101100

∴ Assume 0 to the right of the multiplier LSB.

1 0 1 1 0 0 0 Multiplier
 -1 +1 0 -1 0 0 Recoded Multiplier

2) 0 1 1 0 0 1
 0 1 1 0 0 1 0
 +1 0 -1 0 +1 -1 Recoded Multiplier

* Booth's multiplication:-

Q = Multiplier: 0 0 1 1 0 0 Multiplicand: 0 1 0 0 1 1
 Recoded multiplier: 0 +1 0 -1 0 0

Multiplication:

0	1	0	0	1	1	
0	+1	0	-1	0	0	
0	0	0	0	0	0	0 0 0 0
0	0	0	0	0	0	0 0 0 0
1	1	1	1	1	0	0 1 0 0
0	0	0	0	0	0	0 0 0 0
0	0	0	1	0	0	1 1 0 0
0	0	0	0	0	0	0 0 0 0
0	0	0	0	1	1	0 0 1 0

* Whenever multiplicand is multiplied by -1 its 2's complement is taken as a partial result.
 0 1 0 0 1 1 → 1 0 1 1 0 0
 ← 2's complement of the multiplicand.
 (positive to positive multiplier)

* The same algorithm can be used for negative multiplier.

* Multiply ~~0110~~ 01110 (+14) & 11011 (-5)
 Soln:-

0 1 1 1 0 (+14) Multiplicand
 1 1 0 1 1 (-5) Multiplier
 0 -1 +1 0 -1 Recoded Multiplier

Multiplication:

0	1	1	1	0		
0	-1	+1	0	-1		
1	1	1	1	1	0	0 1 1 0
0	0	0	0	0	0	0 0 0 0
0	0	0	0	0	0	0 0 0 0
1	1	1	0	0	0	0 1 1 0
0	0	0	0	0	0	0 0 0 0
1	1	1	0	1	1	0 1 1 0

0 1 1 1 0
 1 0 0 0 1
 1 0 0 1 0
 ← 2's Complement of the multiplicand.

1 1 1 0 1 1 1 0 1 0 (-70)


same algorithm also can be used for negative multiplier & negative multiplicand.

Multiplicand: 110011 (-3) (-19)



Multiplier: 101100 (-12)

Recoded Multiplier: -1+10-100

Multiplication:

 

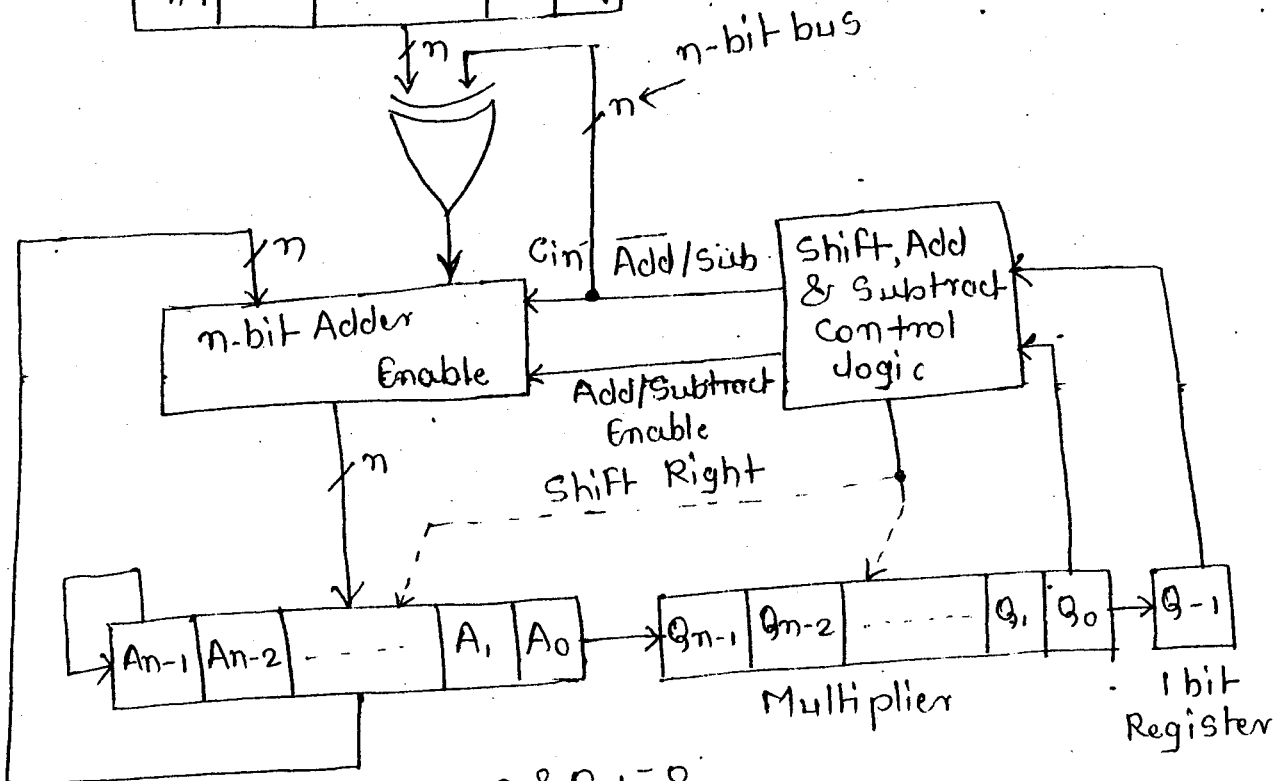 * Implementation of signed binary multiplication:-



* Initial Settings: $A \leftarrow 0$ & $Q_{-1} = 0$

It consists of n -bit adder, Shift, add Subtract control log & four registers, A, B, Q & Q_{-1} . Multiplier & multiplicand are coded into register Q & register B. & register A & Q_{-1} are initially set to 0. Control logic scans the bits of the multiplier.

→ The n -bit adder performs addition of two inputs. One input is the A & other input is multiplicand.

→ In case of addition, Add/Sub line is 0 ∴ $C_{in} = 0$ & multiplicand is directly applied as a second input to the n -bit adder.

→ In case of subtraction, Add/Sub line is 1 ∴ $C_{in} = 1$ & multiplicand is complemented & then applied to the n -bit adder. As a result, the 2's complement of multiplicand is added in the A register.

* Truth table for Shift, add & Subtract control logic:

Q_0	Q_{-1}	Add/Sub	Add/Subtract Enable	Shift
0	0	x	0	1
0	1	0	1	1
1	0	1	1	1
1	1	x	0	1

1) If two bits are same, then all the bits of the A, Q & Q_{-1} registers are shifted to right 1 bit without addition or subtraction (Add/subtract Enable = 0). ($Q_0 = 0, Q_{-1} = 0 \text{ or } 1$)

2) If $Q_0 = 0$ & $Q_{-1} = 1$ then multiplicand is added & if bits are $Q_0 = 1$ & $Q_{-1} = 0$ then multiplicand is subtracted. After addition

* Flowchart: -

Case 1) Both Positive (5x4)

Multiplicand (B) ← 0101 (5) Multiplier (Q) ← 0100 (4)

Steps	A	Q	Q-1	Operation
	0000	0100	0	Initial
Step 1:	0000	0010	0	Shift right
Step 2:	0000	0001	0	Shift right
Step 3:	1011	0001	0	A ← A - B
	1101	1000	1	Shift right
Step 4:	0010	1000	1	A ← A + B
	0001	0100	0	Shift right

Result: 0001 0100 = +20

$$\begin{array}{r} 0101 - 1's \\ 1010 \\ + 1 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} 1101 \\ + 0101 \\ \hline 0010 \end{array}$$

Case 2) Negative Multiplier (5x-4)

Multiplicand (B) ← 0101 (5) Multiplier (Q) ← 1100 (-4)

Steps	A	Q	Q-1	Operation
	0000	1100	0	Initial
Step 1:	0000	0110	0	Shift right
Step 2:	0000	0011	0	Shift right
Step 3:	1011	0011	0	A ← A - B
	1101	1001	1	Shift right
Step 4:	1110	1100	1	Shift right

Result: 1110 1100 = (-20)
(2's complement of +20)

$$\begin{array}{r} 0101 \\ 1010 \\ + 1 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} 0001\ 0100 \\ 1110\ 1011 \\ \hline 111 \end{array}$$

Case 3) Negative Multiplicand (-5x4) -6x3

Multiplicand (B) ← 1011 Multiplier (Q) ← 0100 (4)

Steps	A	Q	Q-1	Operation
	0000	0100	0	Initial
Step 1:	0000	0010	0	Shift right
Step 2:	0000	0001	0	Shift right
Step 3:	0101	0001	0	A ← A - B
	0010	1000	1	Shift right
Step 4:	1101	1000	1	A ← A + B
	1110	1100	0	Shift right

$$\begin{array}{r} 1011 \\ 0100 \\ \hline 0101 \\ 0010 \\ + 1011 \\ \hline 1101 \end{array}$$

Result: 1110 1100 = (-20) (2's complement of +20)

Case 4): (-5×4) Both Negative:

Multiplicand (B) \leftarrow 1011 (-5) Multiplier (Q) \leftarrow 1100 (-4)

Steps	A	Q	Q-1	Operation
	0000	1100	0	Initial
Step 1:	00.00	0110	0	Shift right
Step 2:	0000	0011	0	Shift right
Step 3:	0101	0011	0	$A \leftarrow A - B$
	0010	1001	1	Shift right
Step 4:	0001	0100	1	Shift right

1011
0100

0101

Result: 0001 0100 = +20

* Modified Booth's Algorithm:-

To speed-up the multiplication process in the Booth's algorithm a technique called bit-pair recording is used. It is also called Modified Booth's algorithm.

Table for the bit-pair code for all possible multiplier bit operations:

Multiplier bit-pair		Multiplier bit on the right	Bit-pair Recoded multiplier bit at position j
$j+1$	j	$j-1$	
0	0	0	0
0	0	1	+1
0	1	0	+1
0	1	1	+2
1	0	0	-2
1	0	1	-1
1	1	0	-1
1	1	1	0

* Find the bit pair code for multiplier:

11010

By referring table

Sign extension \rightarrow $\boxed{1}$ 1 1 0 1 0 $\boxed{0}$ Implied 0 to right of LSB

Simply given signed 2's complement numbers using bit pair recoding.

A = 110101 multiplicand (-11)

B = 011011 multiplier (+27) → +10-1+10-1

By referring table

0 1 0 1 1 0 Implied 0 to right of LSB
 Multiplication: +2 -1 -1

110101
 +10-1+10-1

111111001011
 000000000000
 11111001011
 011001011
 1001011

110101
 001010
 001011
 001100
 110101
 0001010
 11011
 110

11111001011
 000000000000
 11111001011
 111001011
 0110101
 111001011
 01101010

* A = 01101 (+13) = Multiplicand = B

B = 11010 (-6) = Multiplier = 3

By referring table

Sign extension → 1 1 1 0 1 0 Implied 0 to right of LSB
 0 0 1 1 0 1 0
 ↓ ↓ ↓
 0 -1 -2

Example given signed 2's complement numbers using bit pair recoding.

A = 110101 multiplicand (-11)

B = 011011 multiplier (+27) → +10-1+10-1

By referring table

Multiplication:

0 1 1 0 1 1 0 [] Implied 0 to right of LSB

+2 -1 -1

1 1 0 1 0 1

+2 -1 -1

0 0 0 0 0 0 0 0 0 0 1 0 1 1

0 0 0 0 0 0 0 0 1 0 1 1

0 0 0 0 0 0 1 0 1 1 1

1 1 0 1 0 1

+10 -1 +10 -1

1 1 1 1 1 1 0 0 1 0 1 1

0 0 0 0 0 0 0 0 0 0 0 0

0 0 0 0 0 0 1 0 1 1

0 0 0 0 0 0 0 0

0 0 0 1 1 0 1 0 1 1

1 1 1 1 1 0 0 1 0 1 1

0 0 0 0 0 0 0 0 0 0

1 1 1 1 1 0 0 1 0 1 1

1 1 1 1 0 0 1 0 1 1

0 1 1 0 1 0 1 1

1 0 0 1 0 1 1

0 0 0 0 1 1 0 1 0 1

1 1 1 0 0 1 0 1 1

0 0 0 0 0 0 0 0 0 0

0 1 1 0 1 0 1

0 1 1 0 1 0 1 0

* A = 01101 (+13) = Multiplicand = B

B = 11010 (-6) = Multiplier = 3

By referring table

Sign extension → 1 1 1 0 1 0 [] Implied 0 to right of LSB

0 0 1 1 -1 +1 1 -1 0

↓ ↓ ↓

0 -1 -2